


Tutorial: Quartz Crystal Oscillators & Phase-Locked Loops

Greg Armstrong (IDT)
Dominik Schneuwly (Oscilloquartz)

April 3rd, 2017


Content

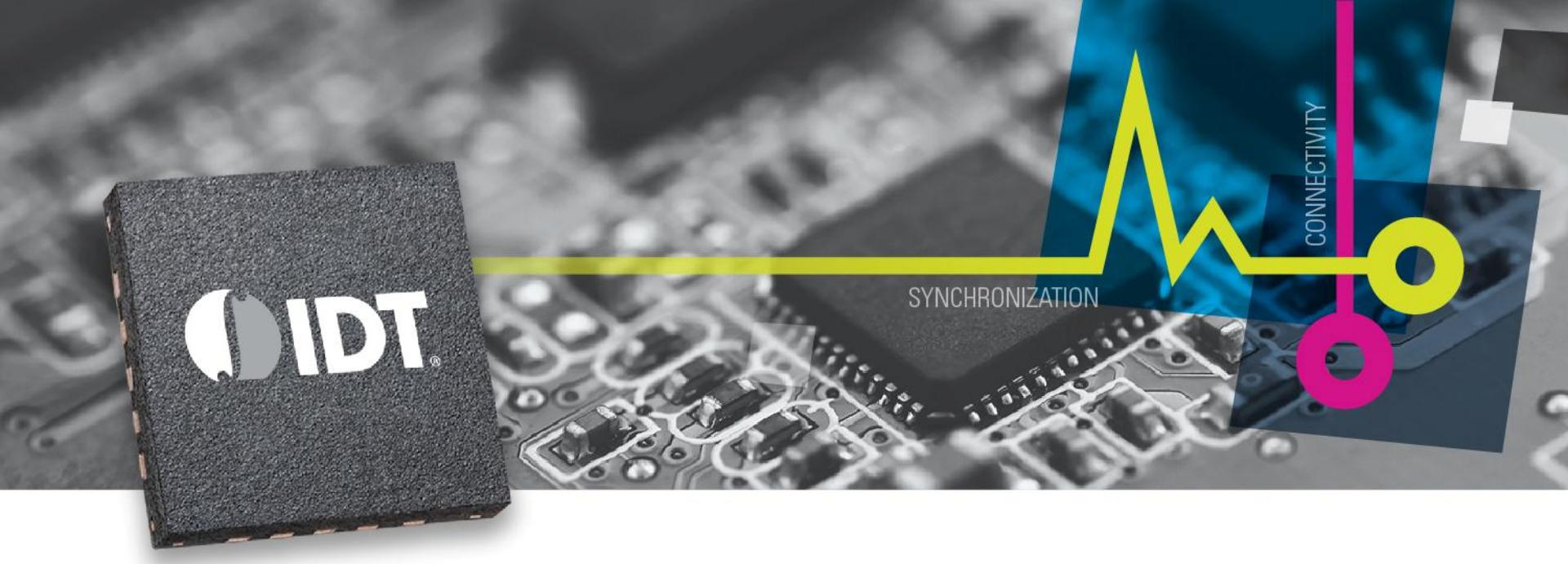1. Quartz Crystal Oscillator (XO) Refresher
2. Phase Locked Loops (PLL)
 - PLL Overview
 - Response To Injected Noise
3. Combining Two PLLs



1. Quartz Crystal Oscillator (XO) Refresher

Frequency Drift Due to Ageing

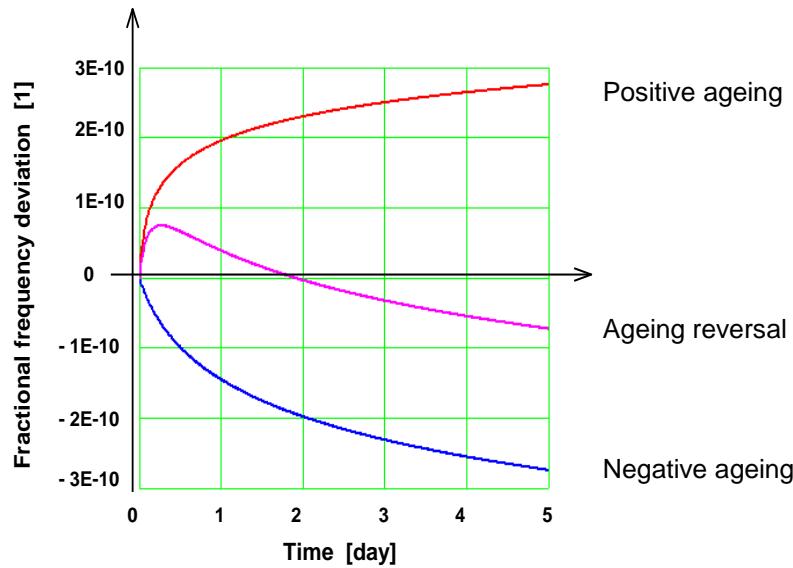

Frequency vs. Temperature


SC-cut:

$$\Theta = 34^\circ$$

$$\Phi = 22^\circ$$



$\Delta f/f$ as a function of temperature
(parameter: $\Delta\Theta$ = deviation from reference angle)

 Lower Turnover Point (LTP)
Inflection Point (IP)
Upper Turnover Point (UTP)




XO Categories rel. Temp. Control

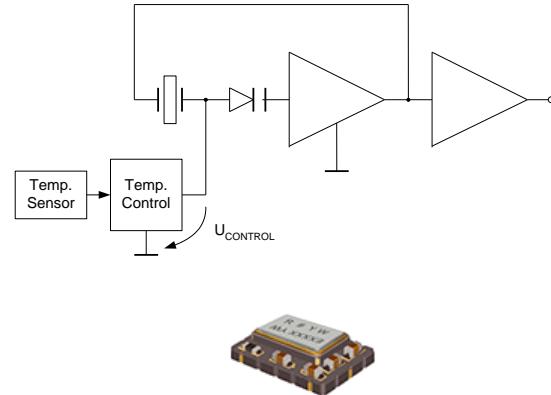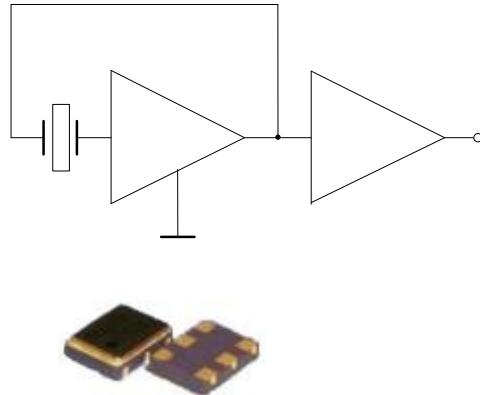- XO, (Uncompensated) Crystal Oscillator:
 - LTP centered in the operation temperature range
 - $> 1E-7 / ^\circ\text{C}$
- TCXO, Temperature Compensated XO:
 - Resonance frequency is modified by a varactor diode so as to compensate temperature sensitivity
 - $5E-8$ to $5E-7$ over $[-55^\circ\text{C} \text{ to } 85^\circ\text{C}]$





XO Categories rel. Temp. Control

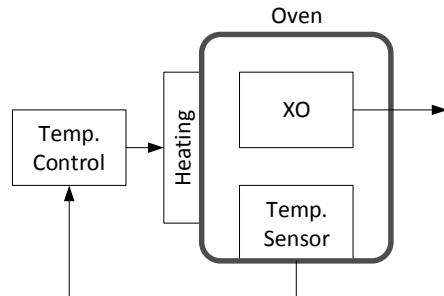- OCXO, Oven Controlled XO:
 - A control loop maintains the oven containing the XO at (nearly) constant temperature.
 - 5E-9 to 5E-8 over [-30°C to 60°C]



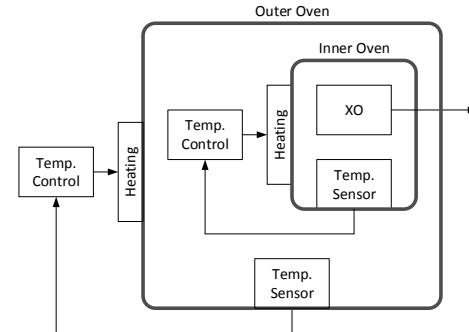
- DOCXO, Double Oven Controlled XO:
 - Two temperature controlled ovens, one inside the other.
 - 5E-11 to 5E-9 over [-30°C to 60°C]



 

2. Phase-Locked Loops (PLL)

PLL: Working principle

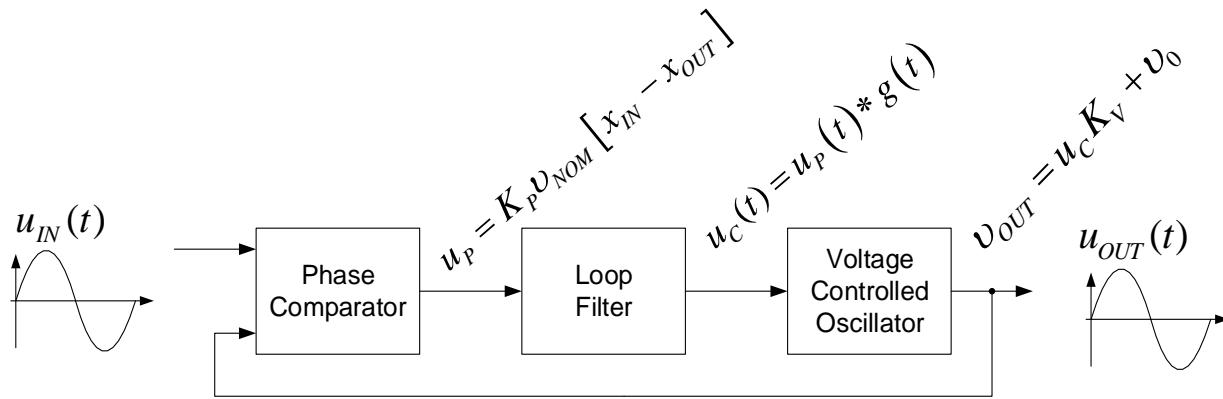


$$u_{IN}(t) = A \cdot \sin \left\{ 2\pi v_{NOM} \left[t + x_{IN}(t) \right] \right\} = A \cdot \sin \left\{ 2\pi v_{IN}(t) + \varphi_{0,IN} \right\}$$

$$u_{OUT}(t) = A \cdot \sin \left\{ 2\pi v_{NOM} \left[t + x_{OUT}(t) \right] \right\} = A \cdot \sin \left\{ 2\pi v_{OUT}(t) + \varphi_{0,OUT} \right\}$$


- A phase lock loop (PLL) is a control system that generates an output signal whose phase is related to the phase of an input signal
 - Bringing the output signal back to the input signal for comparison is called a feedback loop
- By keeping the input and output phase in lock, this implies that the input and output frequencies are the same as well
- PLLs generally generate an output frequency that is a multiple, or even a fractional multiple, of the input frequency
 - May require an integer, or fractional, divider on the feedback
 - May require an integer, or fractional, divider on the input as well

PLL: Phase Comparator

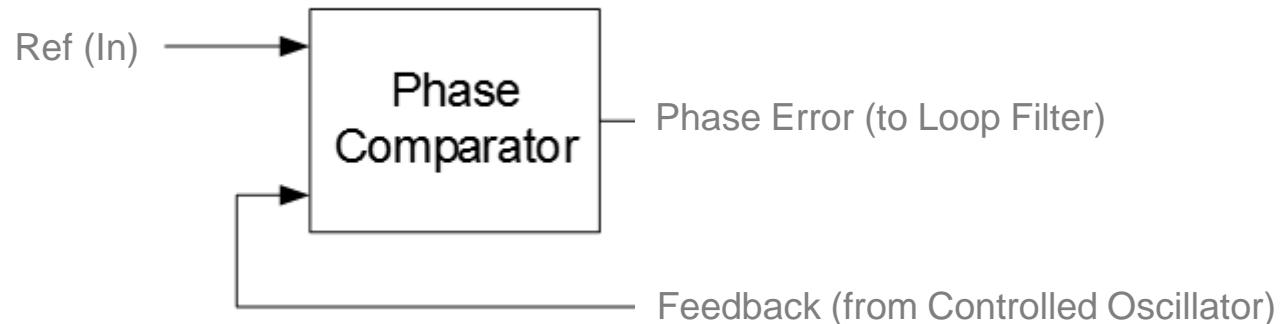


- The Phase Comparator establishes the “error” between the reference input and the clock output; using a feedback
- Most Digital PLLs (DPLLs) use a Time to Digital Converter (TDC) and Phase Frequency Detector (PFD) to measure the phase of the two clocks and produce a digital word representing the error
 - TDC can be looked at as a timestamper
- The TDC timestamps the reference and feedback edges, and the PFD mathematically tracks the phase offset between the selected reference and feedback clocks
- The measured phase difference can go well beyond 1 period, or Unit Interval (UI), of the reference and feedback clocks; thus, the phase comparator must be able to measure over a large range of multiple input/feedback clock periods
 - Various telecom standards define a jitter & wander tolerance requirement - the widest is defined is 18 μ spp
 - For example, if the input clock has a nominal period of 8ns (125 MHz), then the jitter tolerance requirement equates to ± 1125 UI

PLL: Loop Filter

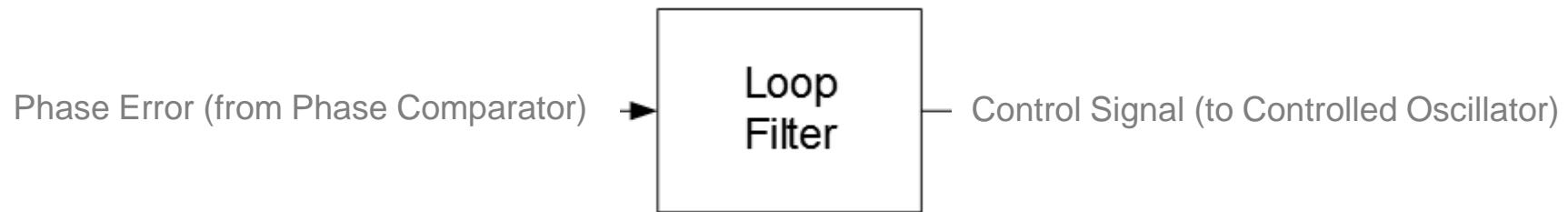



- The phase error is processed by the loop filter (LF)
 - LF is a combination of proportional and integral (PI) control, which generates a control signal for controlling the oscillator
- The LF determines the bandwidth (BW) of the PLL
 - Other functionality, such as phase slope limiting (PSL), locking range, and holdover functionality may be done as well
- Phase corrections mainly done through proportional path, along with any PSL
- Frequency offset, or drift corrections, is done through the integrator path, including damping (i.e. gain peaking control)

PLL: Controlled Oscillator

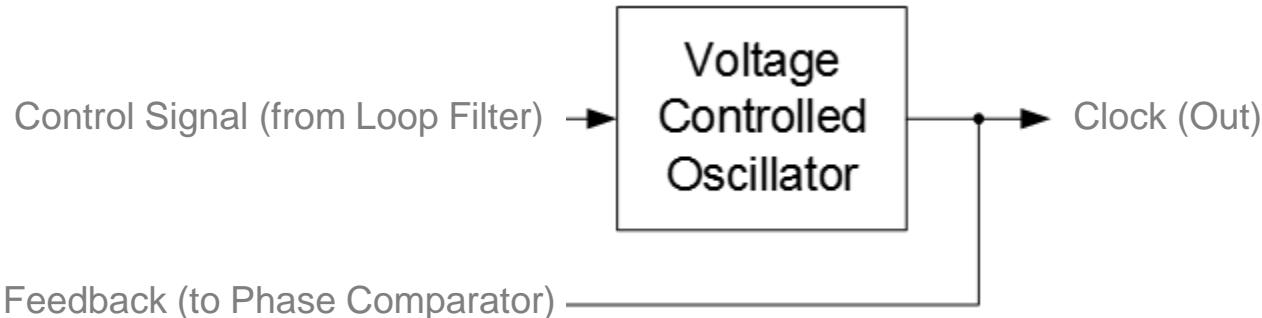


- The controlled oscillator uses the control signal to speed up or slow down the output clock
- Most DPLLs use a Digitally Control Oscillator (DCO) based on a free-running crystal oscillator (XO)
 - Control Signal is a digital word representing the fractional frequency offset (FFO)



PLL: Jitter & Wander filtering

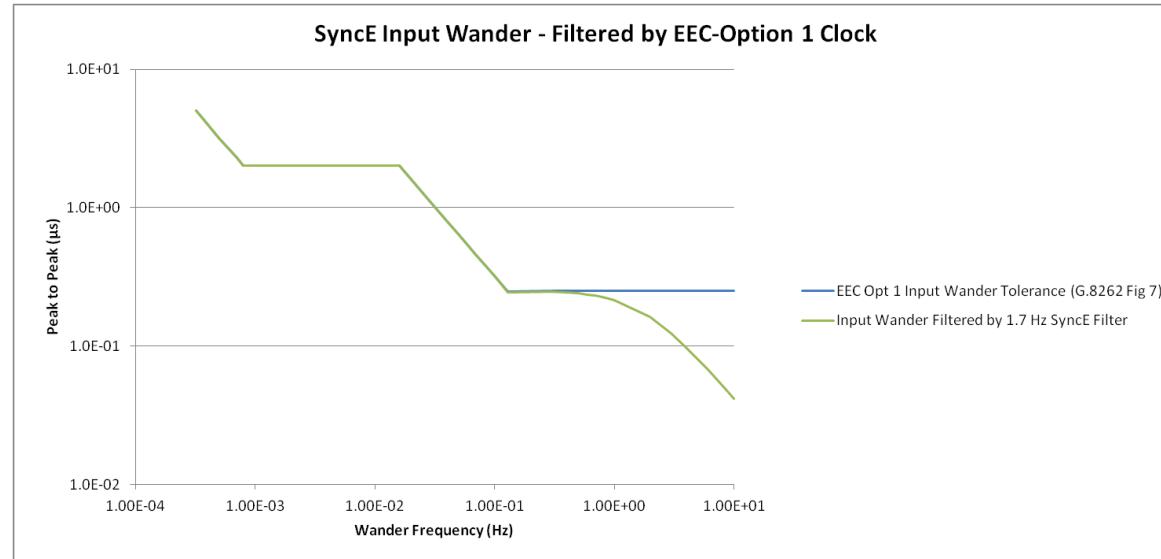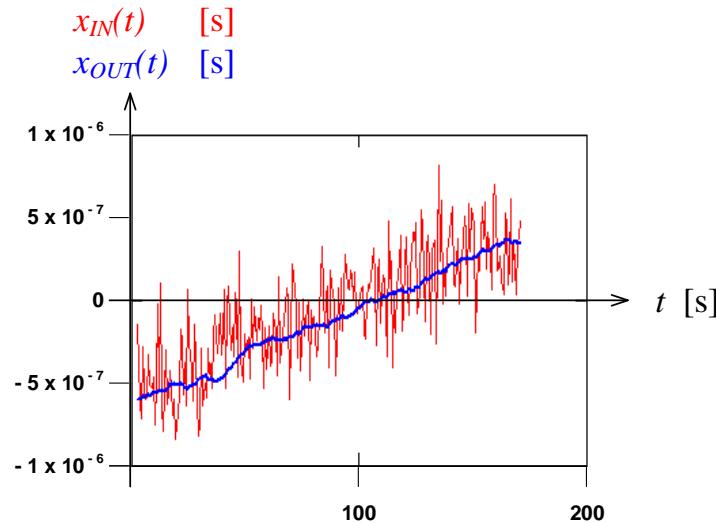


PLL: Response to Injected Noise

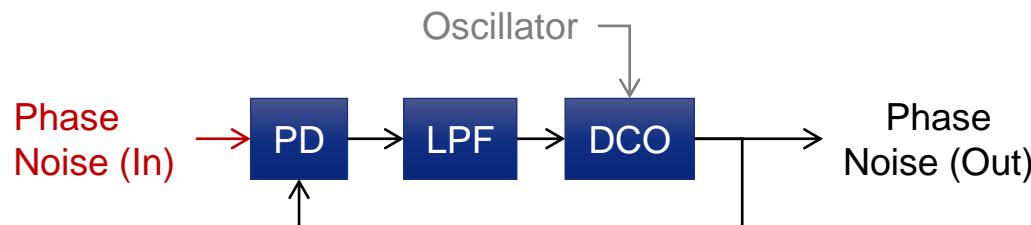


PLL is a low-pass filter for input noise

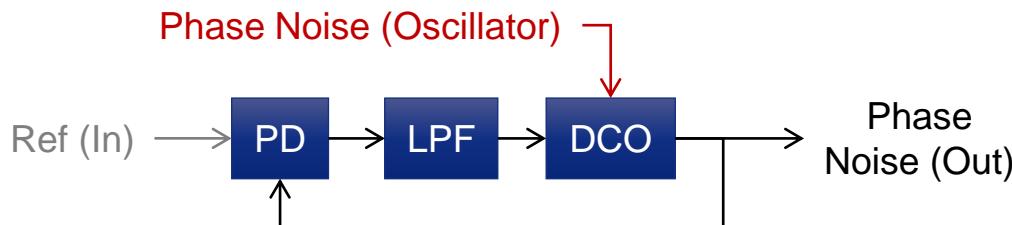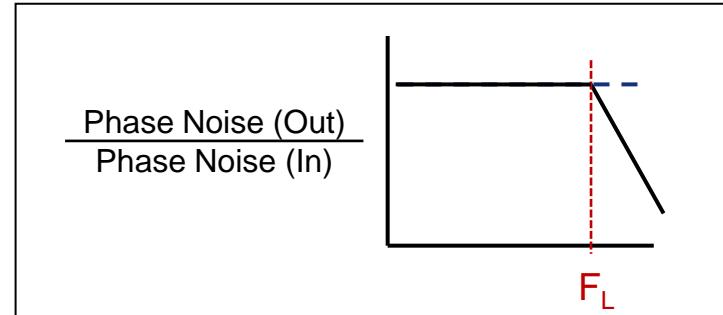



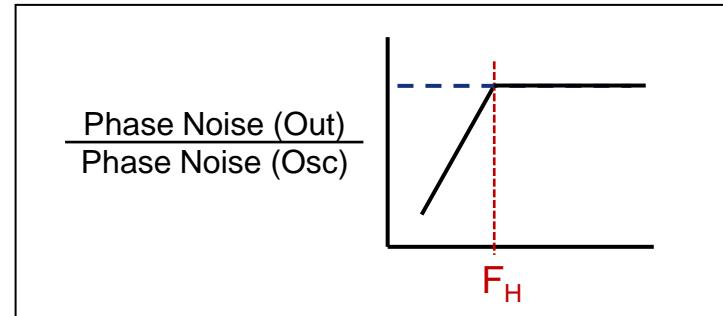
PLL is a high-pass filter for oscillator noise



 


3. PLL with 2 Inputs


Combining two PLLs

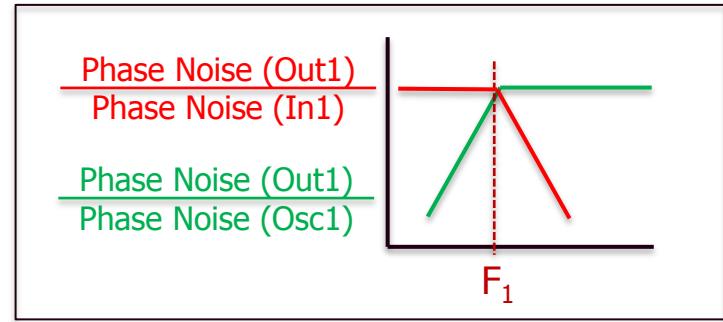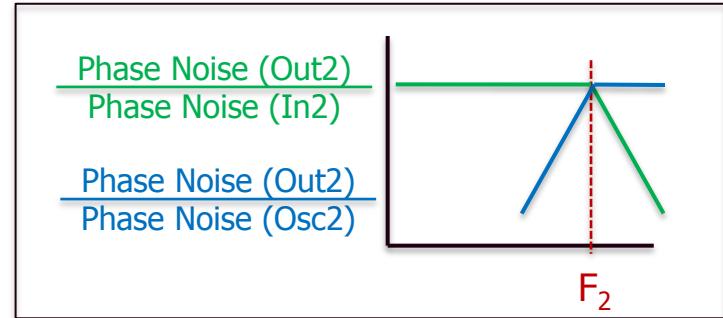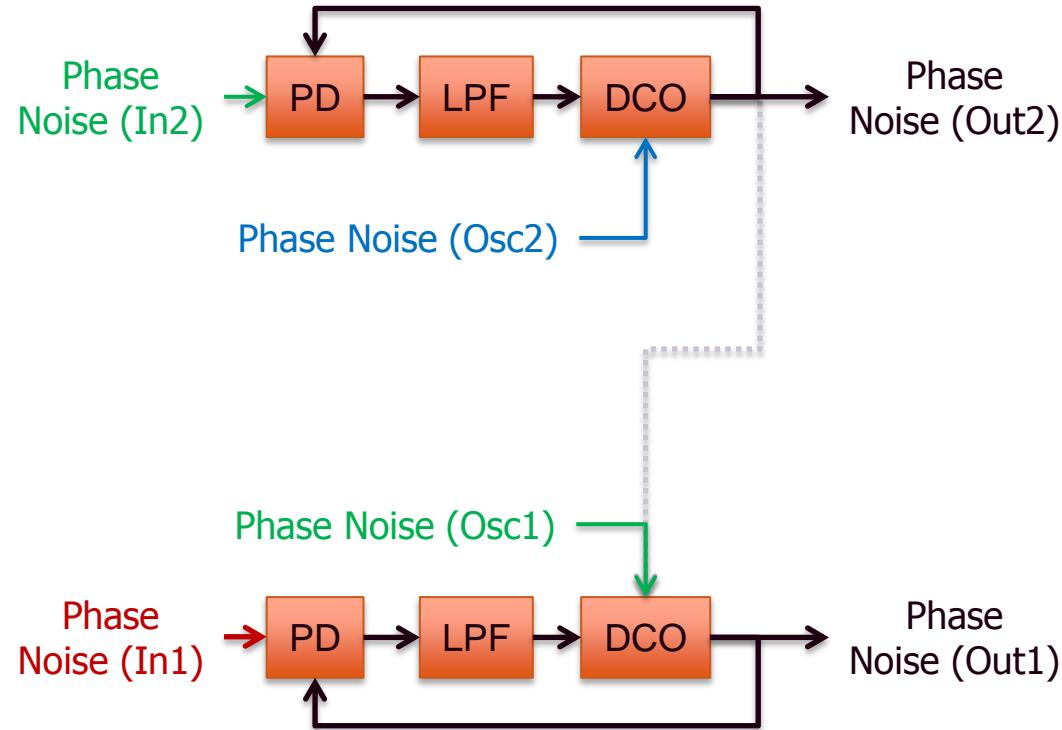


Two PLLs: Response to Injected Noise

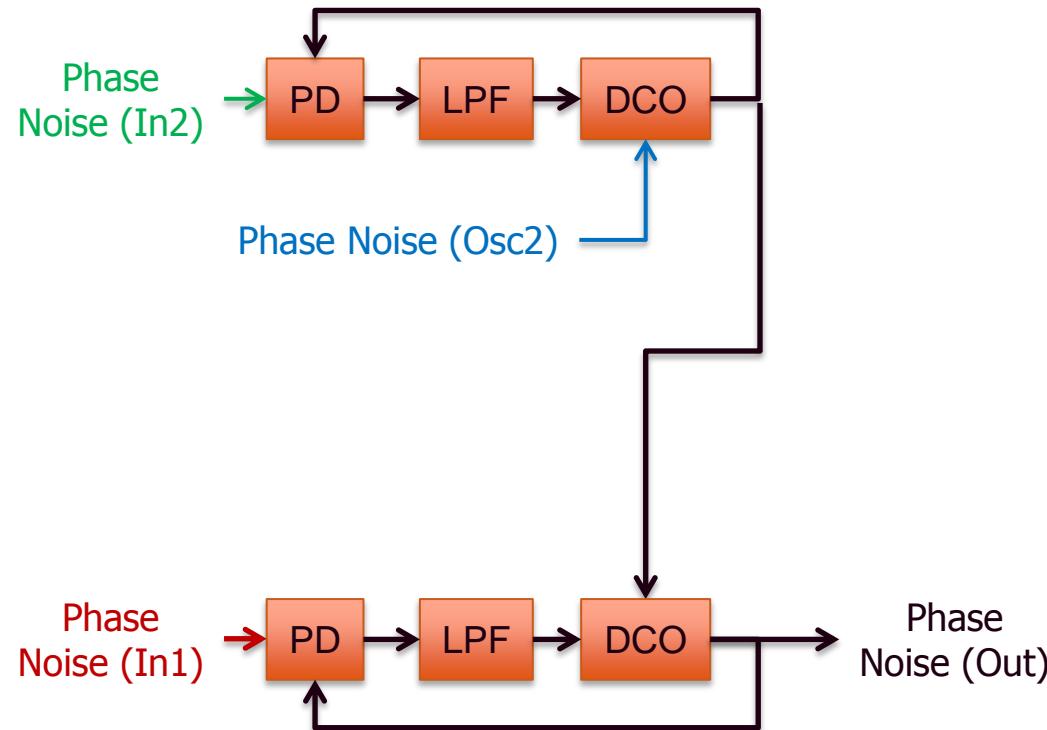


Band-pass filter for In2 Noise to Out

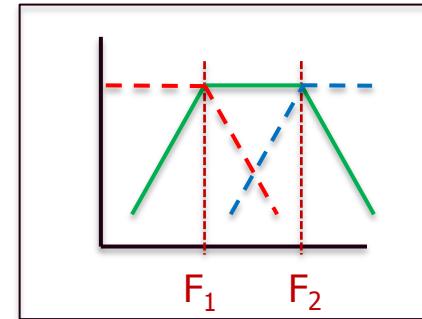

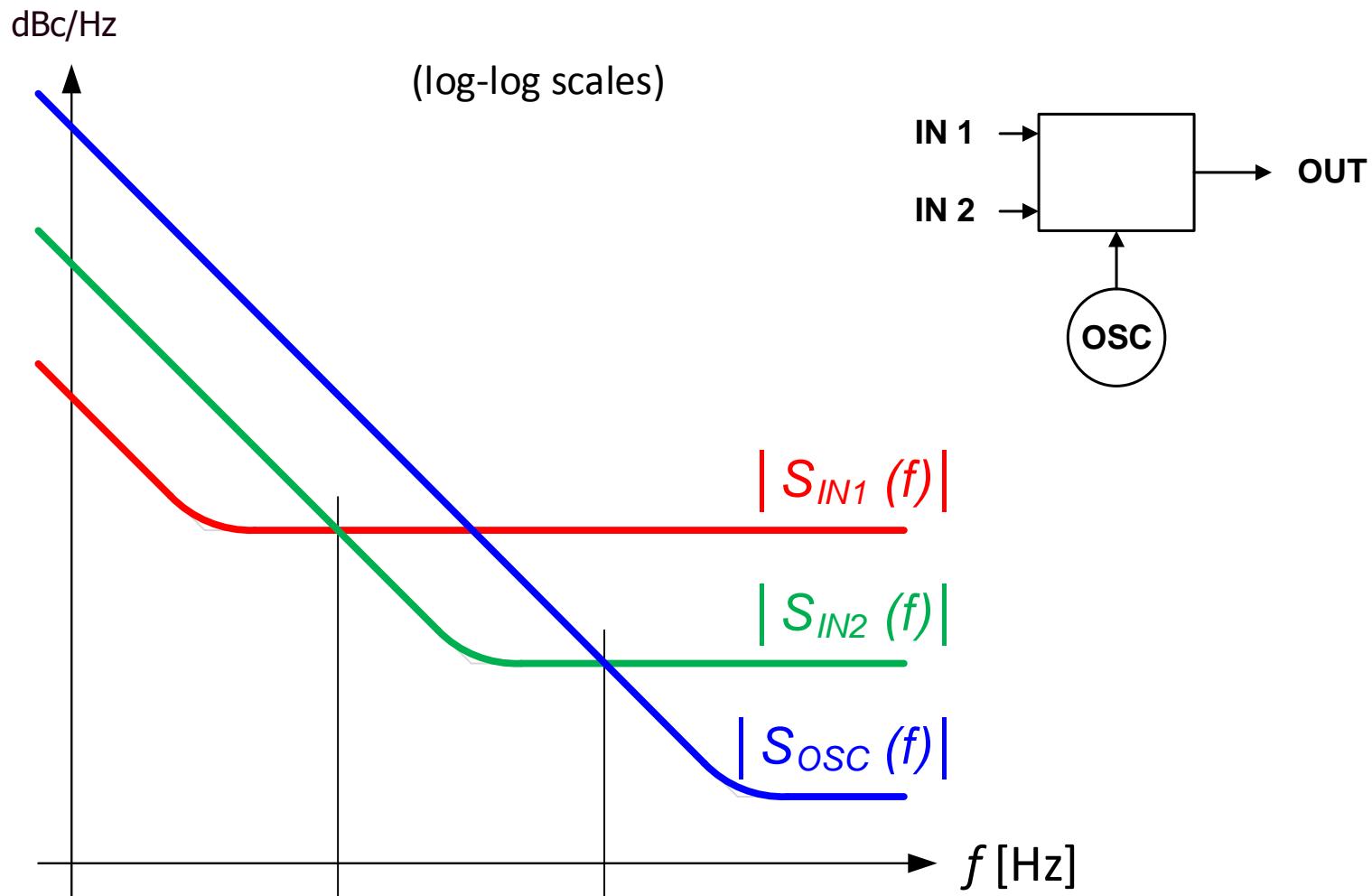Two PLLs: Spectral densities (phase-time)



Two PLLs: Combined spectral densities

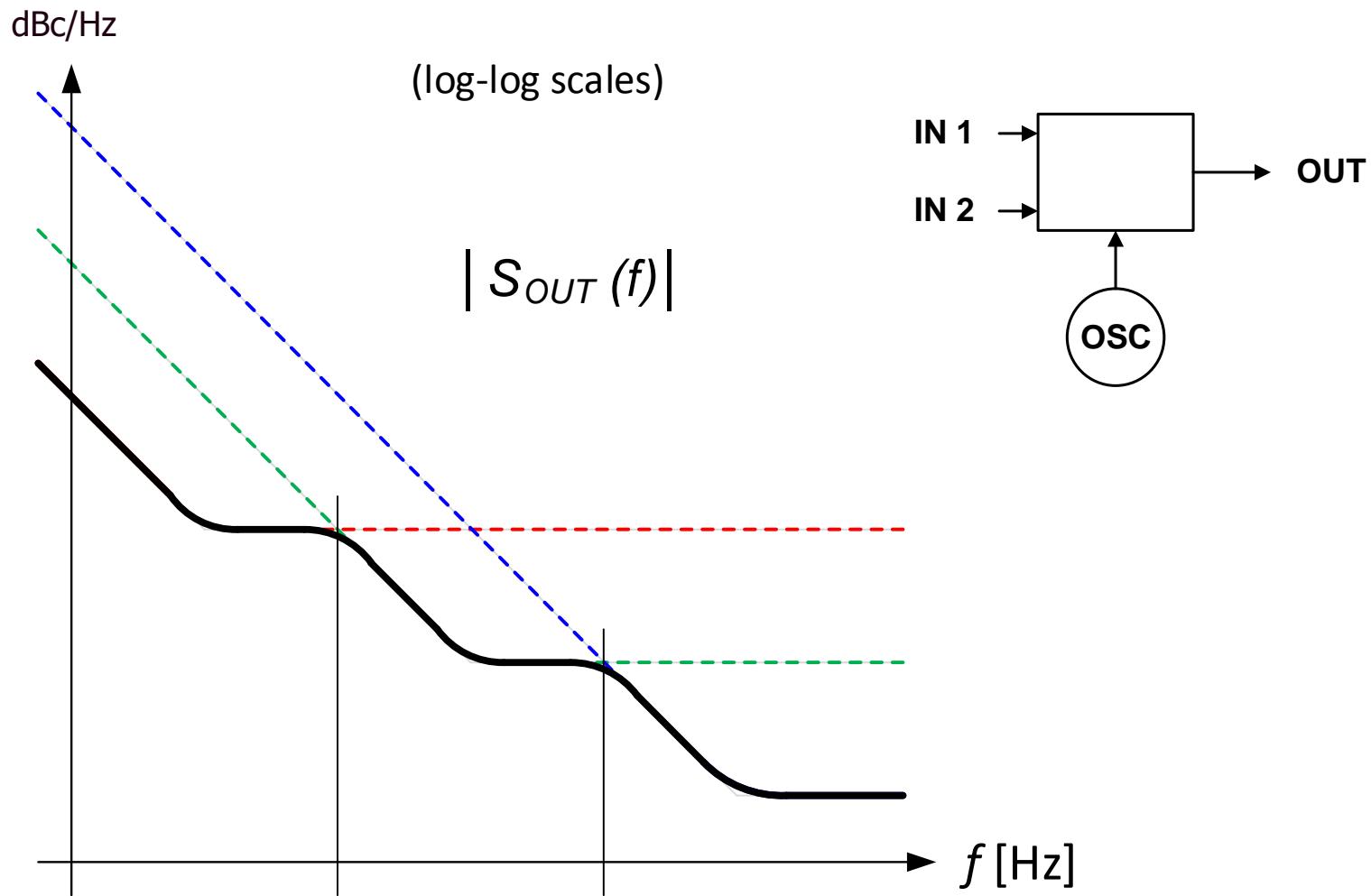

Physical Layer Support for Telecom Boundary Clock

- G.8273.2 calls for Telecom Boundary Clock (T-BC) to use the physical layer as the basis for the frequency of the PTP time clock
- G.8273.2 uses PRC/PRTC traceable physical layer frequency support for long term (24hrs) time holdover



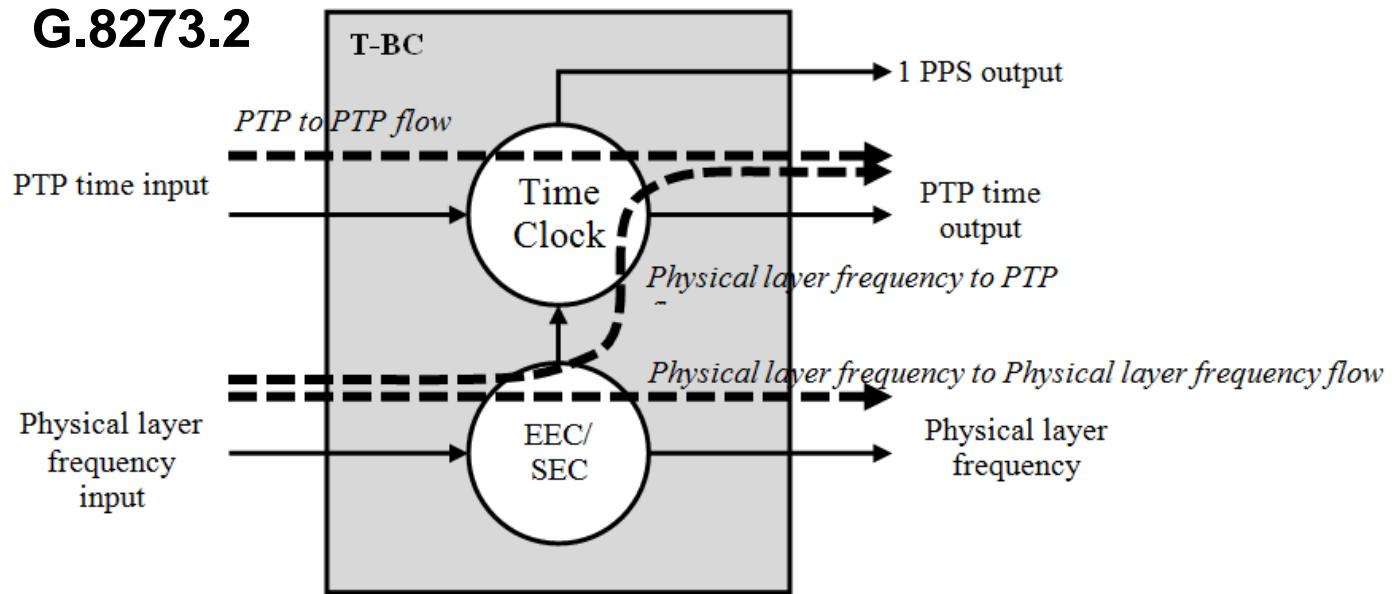


Figure III.5: Signal Flows through a T-BC

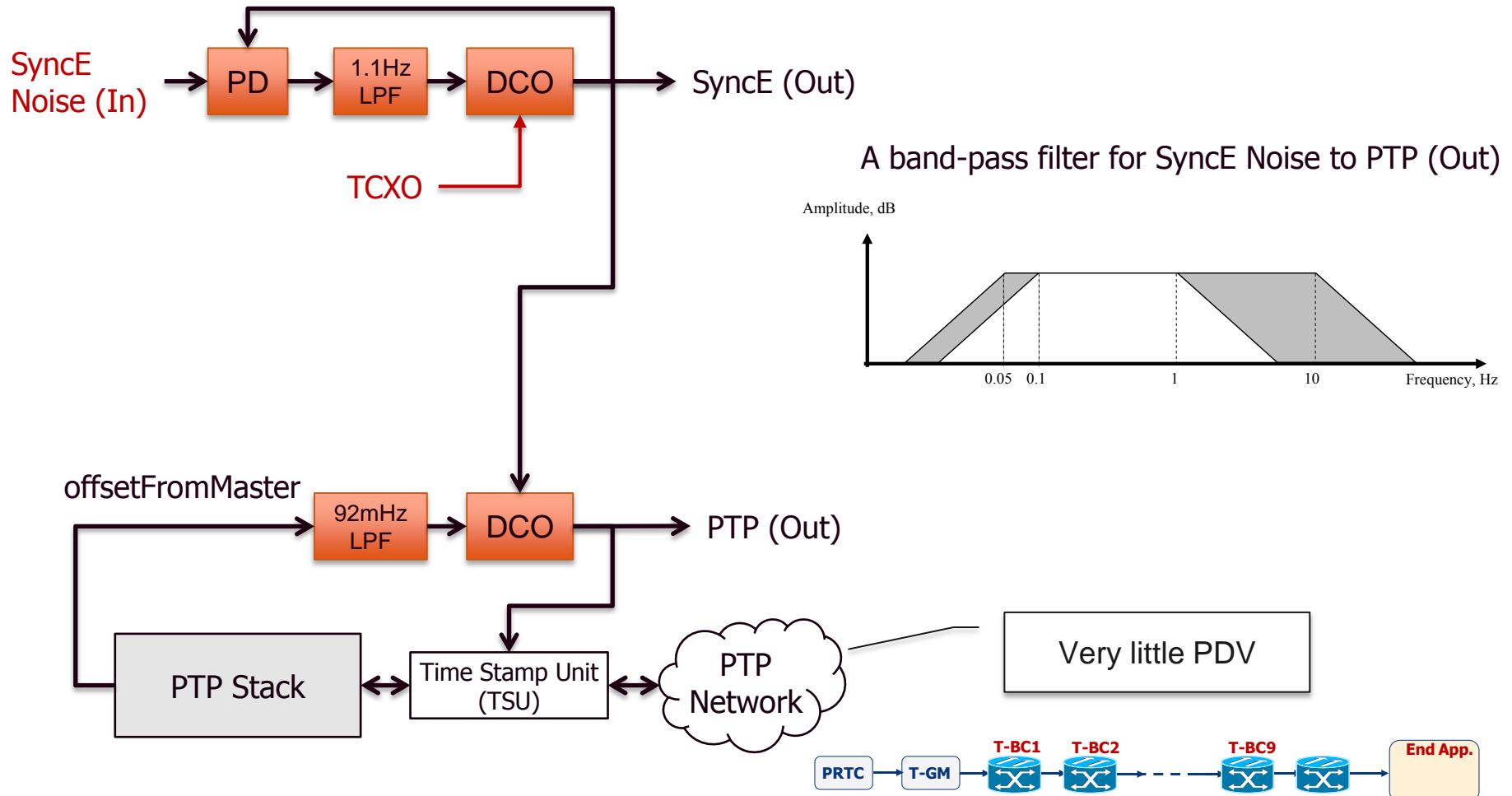SyncE + IEEE 1588: Response to Injected SyncE Noise



 

Thank You

Analog Mixed Signal Product
Leadership in Growth Markets